



Introduction to VHDL V

Finite State Machines - Examples


Roland Höller
Email: hoeller@technikum-wien.at

FSM – Finite State Machine


- Why care about FSMs?
 - They are important building blocks of circuits
 - Their proper operation is most often crucial for the design
 - FSM may be optimized very efficiently by special EDA tools
 - FSMs tend to get quite complex

Finite State Machines

MEALY FSM

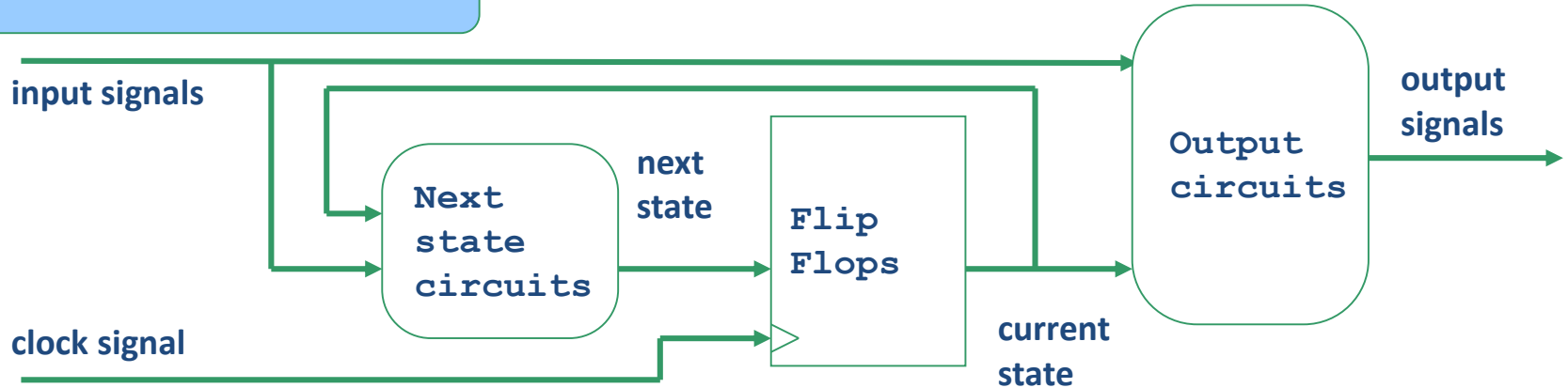

MOORE FSM

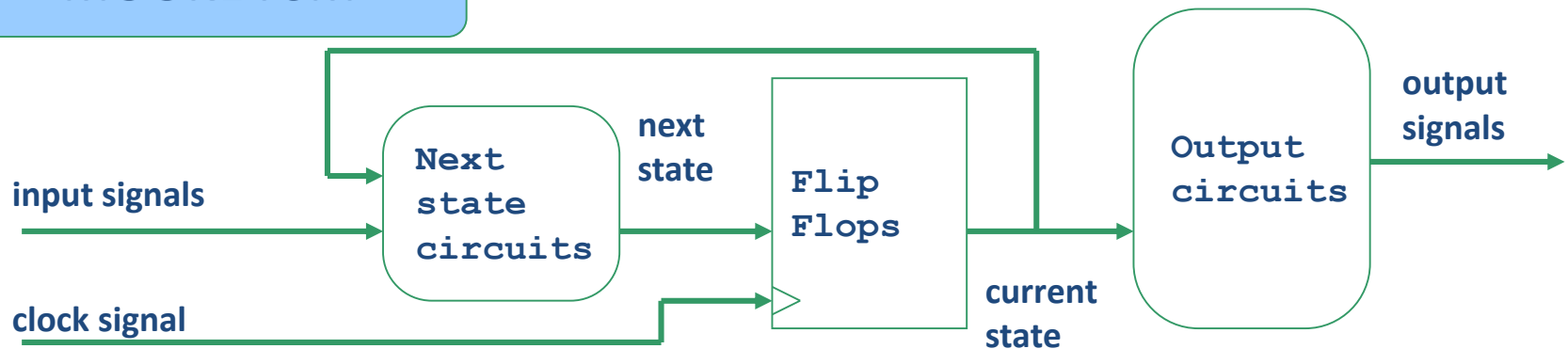


State Vector Representation

- There are different solutions how to specify the state vector and describe the FSM
- By structure:
 - Single sequential process
 - Two processes (sequential and combinatorial)
- By state vector type:
 - enumerated type
 - `std_logic_vector` (binary, one-hot, gray, ...)
 - integer

State Vector Representation

- For the purpose of modeling circuits in VHDL there is actually no big difference
- But there is a difference due to the interpretation of the tools during the design implementation

Example: Traffic Light

 

FSM – One Process

```
type t_state is (red, yellow, green);  
signal s_state : t_state;  
  
begin  
p_fsm : process (clk_i, reset_i)  
begin  
    if (reset_i = '1') then  
        s_state <= red;  
    elsif (clk_i'event and clk_i = '1') then  
        case s_state is  
            when yellow => s_state <= red;  
            when green  => s_state <= yellow;
```

FSM – One Process

```
when others =>  
    if (s_button_i = '1') then  
        s_state <= green;  
    end if;  
end case;  
end if;  
end process p_fsm;
```


FSM – One Process

- Advantages
 - Enhanced readability (RTL only)
 - Eases code debugging
 - Enables technology specific optimization during synthesis
- Disadvantages
 - No control of implementation
 - After synthesis the enumerated type will be converted to a `std_logic_vector` type

FSM – Two Processes

```
type t_state is (red,yellow,green);  
signal s_present_state : t_state;  
signal s_next_state    : t_state;  
  
begin  
p_fsm_seq : process (clk_i,reset_i)  
begin  
    if (reset_i = '1') then  
        s_present_state <= red;  
    elsif (clk_i'event and clk_i = '1') then  
        s_present_state <= s_next_state;  
    end if;  
end process p_fsm_seq;
```

FSM – Two Processes

```
p_fsm_comb : process(s_present_state,s_button_i)
begin
  case s_present_state is
    when yellow =>
      s_next_state <= red;
    when green =>
      s_next_state <= yellow;
    when others =>
      if (s_button_i = '1') then
        s_next_state <= green;
      else                                -- required to avoid
        s_next_state <= red; -- latch insertion !!
      end if;
  end case;
end process p_fsm_comb;
```

FSM – Two Processes

- Advantages
 - Most general description of an FSM
 - Both Mealy and Moore type FSMs may be implemented
- Disadvantages
 - More code to write
 - Required complete sensitivity list
 - Sometimes less readable

FSM – Integer Subtype

```
subtype t_state is integer range 0 to 2;
signal s_state : t_state;

begin
p_fsm : process (clk_i, reset_i)
begin
    if (reset_i = '1') then
        s_state <= 0;
    elsif (clk_i'event and clk_i = '1') then
        case s_state is
            when 1 => s_state <= 0;
            when 2 => s_state <= 1;
```

FSM – Integer Subtype

```
when others =>  
    if (s_button_i = '1') then  
        s_state <= 2;  
    end if;  
end case;  
end if;  
end process p_fsm;
```

FSM – Integer Subtype

- Advantages
 - Somewhat easier to define
 - Some control of implementation
- Disadvantages
 - Code is less readable
 - Disables technology specific optimization during synthesis
 - After synthesis the enumerated type will be converted to a `std_logic_vector` type

FSM – Binary Encoding

```
signal s_state : std_logic_vector(1 downto 0);

begin
p_fsm : process (clk_i, reset_i)
begin
    if (reset_i = '1') then
        s_state <= "00";
    elsif (clk_i'event and clk_i = '1') then
        case s_state is
            when "01" => s_state <= "00";
            when "10" => s_state <= "01";
```


FSM – Binary Encoding

```
when others =>
    if (s_button_i = '1') then
        s_state <= "10";
    end if;
end case;
end if;
end process p_fsm;
```

FSM – One-Hot Encoding

```
signal s_state : std_logic_vector(2 downto 0);  
  
begin  
p_fsm : process (clk_i, reset_i)  
begin  
    if (reset_i = '1') then  
        s_state <= "000";  
    elsif (clk_i'event and clk_i = '1') then  
        case s_state is  
            when "010" => s_state <= "001";  
            when "100" => s_state <= "010";  
        end case;  
    end if;  
end process;  
end;
```

FSM – One-Hot Encoding

```
when others =>
    if (s_button_i = '1') then
        s_state <= "100";
    end if;
end case;
end if;
end process p_fsm;
```

FSM – Binary / One-Hot Encoding

- Advantages
 - Somewhat easier to define
 - Full control of implementation
 - Same encoding on RTL and post synthesis/layout
- Disadvantages
 - Code is less readable
 - Disables technology specific optimization during synthesis

Summary

- Moore Finite State Machine
- Mealy Finite State Machine
- VHDL Examples

Questions

- 1) Which encodings can be used to represent the state vector of an FSM?
 - A binary
 - B gray
 - C one-hot
 - D “0001” -> “0011” -> “0111” -> “1111”-> “0001” -> ...
- 2) What is an automaton called, whose outputs are a function of the state vector only?
 - A Moore
 - B Mealy
 - C secure
 - D minimal
- 3) Which VHDL data type is best used for encoding the state vector of a complex FSM?
 - A integer
 - B real
 - C enumeration type
 - D bit_vector

Class Example: 4-bit Shift Register

1) Describe and simulate a D- Flip Flop in VHDL

2) Add the shift capability to the VHDL code

en_i	sh_i	q_o
0	0	hold
0	1	hold
1	0	d_i -> q_o
1	1	shift left of q_o

