




Introduction to VHDL I

Motivation – Entity – Architecture – Components -
Instantiation - Examples

Roland Höller
Email: hoeller@technikum-wien.at


Motivation – First Transistor

 

[Source: e&i 7/8/1998 S. 345, Springer Verlag, Wien]

- 16th December 1947:
first transistor
- (Bardeen, Brattain and
- Shockley - Bell Labs)


Motivation – First IC

 

[Source: e&i 7/8/1998 S. 345, Springer Verlag, Wien]

- One of the first ICs (Flip-Flop)


Motivation – State of the Art IC

 

- Modern Microprocessor (Intel Core):
 - approx. $1.4 \cdot 10^7$ transistors,
 - 22 nm CMOS technology,
 - 3-D Tri-Gate transistors

[Source: <http://www.intel.com/content/www/us/en/history/history-intel-chips-timeline-poster.html>]

Motivation - Moore's Law

 


[Source: <http://www.intel.com/content/www/us/en/history/history-intel-chips-timeline-poster.html>]

Motivation

Nowadays ASICs face:

 - growing system complexity
- SoC
- ever shrinking time to market
- design reuse
- verification
- quality and reliability
- documentation



VHDL History




- early '70s: Initial discussion
- late '70s: Definition of requirements
- mid - '82: Contract of development with IBM, Intermetrics and TI
- mid - '86: IEEE-Standard
- 1987: DoD adopts the standard
IEEE Std 1076-1987
- mid - '88: Increasing support by EDA tools
- late '91: Revision
- 1993: New standard IEEE Std 1076-1993
- 1999: VHDL-AMS IEEE Std 1076.1-1999
- 2000: New standard IEEE Std 1076-2000

VHDL Application Field

- IC Design (digital)
 - specification and documentation
 - modelling of digital systems
 - simulation with testbenches
 - ASIC-, FPGA-, CPLD-design
 - softcores
 - hardware/software co-design

HDL Design Flow

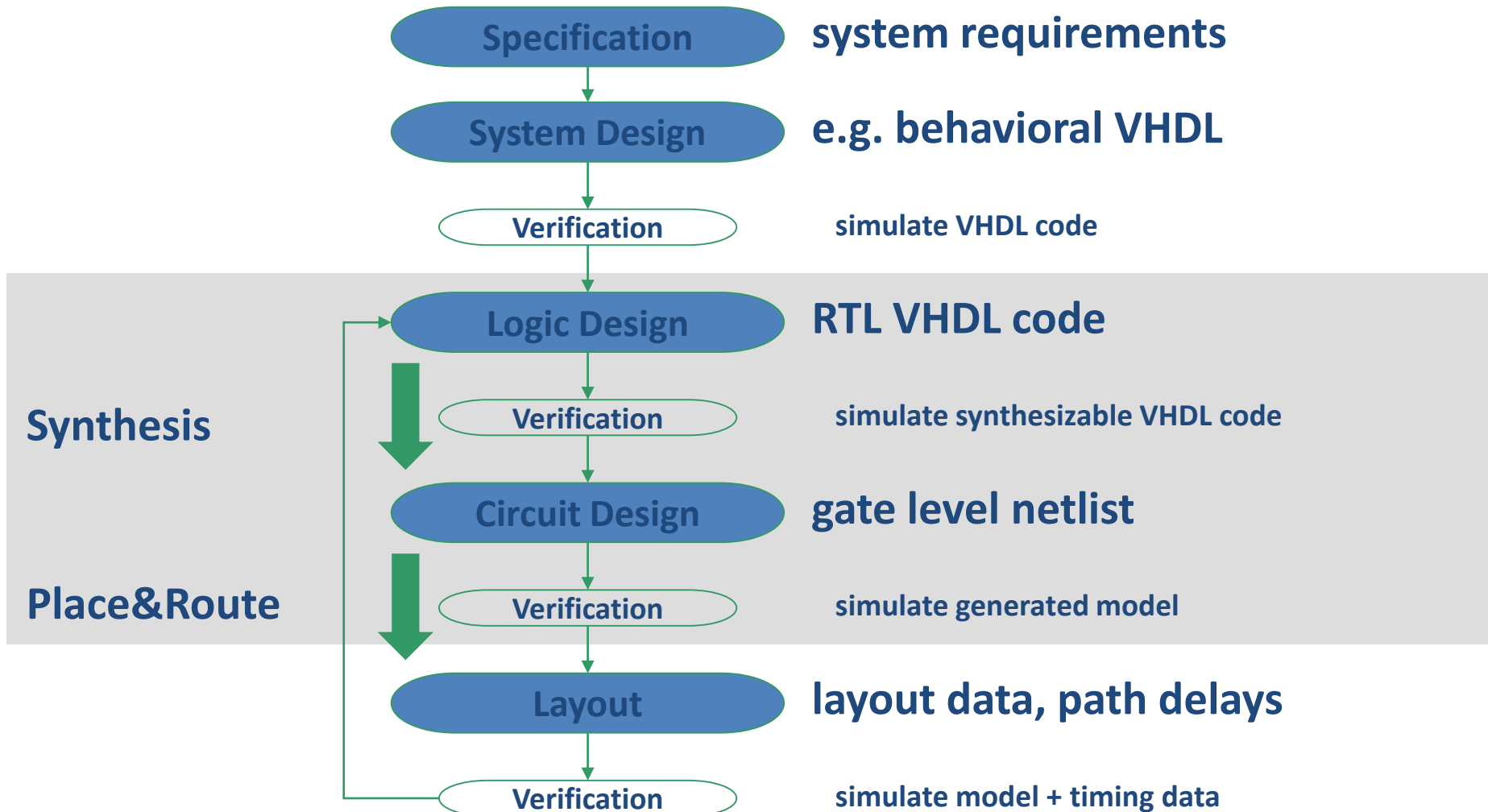


Levels of Abstraction


Behavioral Level




Register Transfer Level

 


Gate Level

 

Layout Level

 

Information in Abstraction Levels

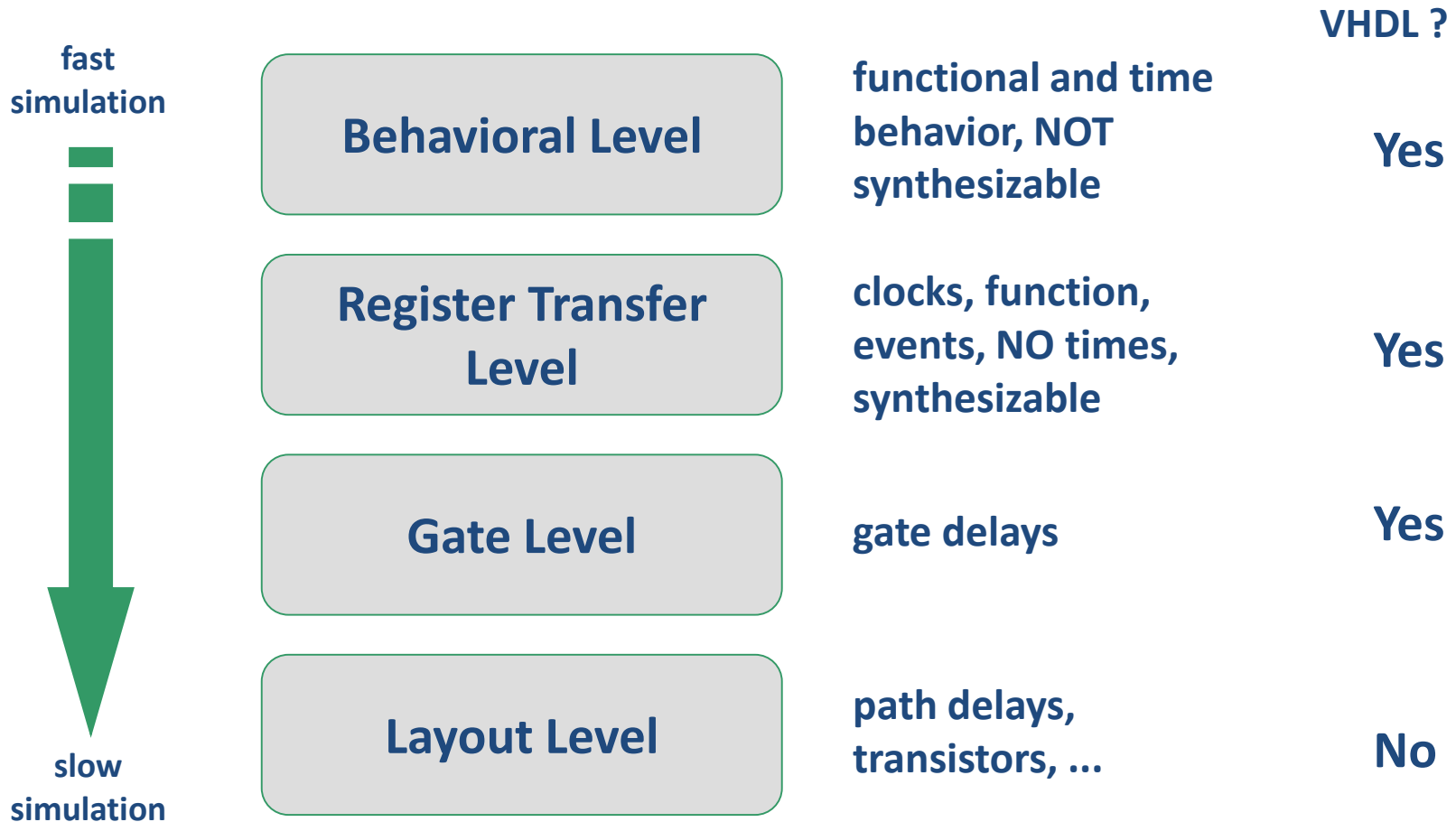

VHDL Overview I

- VHDL properties
 - modelling of digital systems
 - man- and machine-readable specification
 - implies documentation
 - man- and machine-readable documentation
 - transportability
 - simulateable source code
 - strong type oriented, not case sensitive
 - concurrent and sequential statements

VHDL Overview II

- International Standards
 - IEEE Std 1076-1987
 - IEEE Std 1076-1993
 - IEEE Std 1076.1-1999 (AMS)
 -
 - IEEE Std 1076.6-1999 (RTL Synthesis)
 - IEEE Std 1076-2000 (LRM)
- Pure definition in the LRM
 - Language Reference Manual
 - No standards for application or methodology!


VHDL Constructs (VHDL 87/93/00)

- Entity: unit interface
- Architecture: unit behaviour, function
- Configuration: connects entity-architecture pairs
- Library: organize design units
- Package: data types, constants, components
- Process: concurrent, event controlled
- Block: concurrent, group assignments

The Entity

- Interface description
- No behavior or function
- Linking via ports (in, out, inout)
- Declared once within a design
 
```
entity halfadder is
    port (a_i : in std_logic;
          b_i : in std_logic;
          sum_o : out std_logic;
          cy_o : out std_logic);
end halfadder;
```




The Architecture

- Implementation of the design
- Describes circuitry or function
- Different architectures for one entity

```
architecture rtl of halfadder is
begin
    sum_o <= a_i xor b_i;
    cy_o  <= a_i and b_i;
end rtl;
```

Coding Styles:

- rtl
- behavioral
- structural
- sim

 

Circuit Representations

```
architecture rtl of halfadder is
```

```
begin
```

```
    sum_o <= a_i xor b_i;
```

```
    cy_o  <= a_i and b_i;
```

```
end rtl;
```

```
architecture behavioral of halfadder is
```

```
begin
```

```
    sum_o <= a_i xor b_i after 5 ns;
```

```
    cy_o  <= a_i and b_i after 4 ns;
```

```
end behavioral;
```

```
architecture structural of halfadder is
```

```
begin
```

```
    i_xor_gate : xor_gate
```

```
        port map (opa_i => a_i,
```

```
                  opb_i => b_i,
```


```
                  res_o => sum_o);
```

```
end structural;
```

The Configuration

- Declaration of entity-architecture pairs for simulation
- Default configuration is most recently analyzed
- Non-default configuration sometimes necessary
- Entity and component names are identical (default)

 
```
configuration halfadder_rtl_cfg of
halfadder is
  -- architecture rtl is used
  -- for entity halfadder
  for rtl
  end for;
end halfadder_rtl_cfg;
```



The Component Declaration

- In advance of usage in an architecture
- Comparable to a „socket“

 
```
architecture struct of fulladder is
  component halfadder
    port (a_i    : in  std_logic;
          b_i    : in  std_logic;
          cy_o    : out std_logic;
          sum_o   : out std_logic);
  end component;
begin
```



The Component Instantiation

- Wiring of the modules
- After architecture begin
 
```
begin
u1 : halfadder
  port map
    (a_i    => a_i,
     b_i    => b_i,
     cy_o   => s_cy1,
     sum_o  => s_sum1);
```



The Half Adder

```
entity halfadder is
    port (a_i :    in  std_logic;  -- operand a
          b_i :    in  std_logic;  -- operand b
          sum_o : out std_logic;  -- sum of a and b
          cy_o :  out std_logic); -- carry
end halfadder;

architecture rtl of halfadder is
begin
    -- generate the output sum_o
    sum_o <= a_i xor b_i;
    -- generate the output cy_o
    cy_o  <= a_i and b_i;
end rtl;

configuration halfadder_rtl_cfg of halfadder is
    -- architecture rtl is used
    -- for entity halfadder
    for rtl
    end for;
end halfadder_rtl_cfg;
```

The Or Gate

```
entity orgate is
  port (a_i :    in  std_logic;  -- operand a
        b_i :    in  std_logic;  -- operand b
        or_o :   out std_logic); -- output
end orgate;

architecture rtl of orgate is
begin
  -- generate the output or_o
  or_o <= a_i or b_i;
end rtl;

configuration orgate_rtl_cfg of orgate is
  -- architecture rtl is used
  -- for entity orgate
  for rtl
  end for;
end orgate_rtl_cfg;
```

The Full Adder I

```
entity fulladder is  
    port (a_i :    in   std_logic;  -- operand a  
          b_i :    in   std_logic;  -- operand b  
          cy_i :    in   std_logic;  -- carry input  
          cy_o :    out std_logic;  -- carry output  
          sum_o :    out std_logic); -- output  
end fulladder;
```

architecture structural **of** fulladder **is**

```
    component halfadder  
        port (a_i    : in   std_logic;  
              b_i    : in   std_logic;  
              cy_o    : out std_logic;  
              sum_o   : out std_logic);  
    end component;
```

The Full Adder II

```
component orgate
    port (a_i   : in  std_logic;
          b_i   : in  std_logic;
          or_o  : out std_logic);
end component;

signal s_sum1 : std_logic;
signal s_cy1  : std_logic;
signal s_cy2  : std_logic;

begin

u1 : halfadder
    port map                                -- named association
        (a_i   => a_i,
         b_i   => b_i,
         cy_o  => s_cy1,
         sum_o => s_sum1);
```


The Full Adder III

```
u2 : halfadder
  port map
    (a_i    => s_sum1,
     cy_o    => s_cy2,
     b_i    => cy_i,
     sum_o   => sum_o);
```

named association:
- independent of order
- more readable

```
u3 : orgate
  port map
    (s_cy2, s_cy1, cy_o);
```

positional association:
- order defines connection
- less readable

```
end structural;
```

```
configuration fulladder_struc_cfg of fulladder is
  -- architecture structural is used
  -- for entity fulladder
  for structural
  end for;
end fulladder_struc_cfg;
```

incomplete configuration
- just binds E/A for top level
- relies on MRA for subunits

Summary

- Motivation
- Design Flow
- Abstraction Levels
- VHDL Overview
- Entity
- Architecture
- Configuration
- Component Declaration
- Example : Full Adder

Questions

- 1) VHDL is used in which phases of a digital circuit design flow?
 - A ASIC-, FPGA-, or PLD-Design only
 - B Description of a system before partitioning into hardware and software
 - C Description of hardware only
 - D All of the abovementioned items
- 2) Which statements are correct?
 - A VHDL is perfectly suited for the description of analog systems
 - B Different synthesis tools support different VHDL language subsets
 - C For the description of a testbench, VHDL coding on RTL is mandatory
 - D All VHDL code, that can be simulated, can also be synthesized
- 3) How many architectures can be associated with a VHDL entity?
 - A One or more
 - C Exactly one
 - B More than one
 - D None
- 4) In which part of a VHDL architecture do signals have to be declared, that shall only be visible locally in that architecture?
 - A In the port list of the corresponding entity
 - C In the architecture after the begin
 - B In the corresponding configuration
 - D In the architecture before the begin
- 5) What do the entity and the corresponding component declaration in most of the cases have in common?
 - A Nothing
 - C Entity and Component different names, but the same ports
 - B Entity and Component have the same name, but different ports
 - D Entity and Component the same name and the same ports

Class Example: AND 2 data busses

1) Create and simulate the design



```
library IEEE;
use IEEE.std_logic_1164.all;
```

```
entity vectorgates is
    port (a_i :    in  std_logic_vector(31 downto 0);    -- operand a
          b_i :    in  std_logic_vector(31 downto 0);    -- operand b
          d_o :    out std_logic_vector(31 downto 0));    -- output
end vectorgates;
```

```
architecture rtl of vectorgates is
begin
    -- generate the output d_o
    d_o <= a_i and b_i;
end rtl;
```

2) „AND“ high word and „OR“ low word

3) Add c_i, d_i of type std_logic and
“XOR” them to the output e_o.